



# EECS 1010 01

# Combinational Logic

黃稚存



國立清華大學  
資訊工程學系

Lecture 04-1

# Outline

- ◉ Introduction
  - ◆ Combinational Circuits
  - ◆ Analysis Procedure
  - ◆ Design Procedure
- ◉ Binary Adder-Subtractor
- ◉ Decimal Adder
- ◉ Binary Multiplier
- ◉ Magnitude Comparator
- ◉ Decoder and Encoder
- ◉ Multiplexer
- ◉ Three-State Gates

# Objectives

- ◉ Know how to analyze a combinational logic circuit, given its logic diagram
- ◉ Understand the half-adder and full-adder
- ◉ Understand the overflow and underflow
- ◉ Understand the implementation of a binary adder, BCD adder, and binary multiplier
- ◉ Understand fundamental combinational logic circuits: decoder, encoder, priority encoder, multiplexer, and three-state gate


# Introduction

- » Combinational Circuits
- » Analysis Procedure
- » Design Procedure

# Logic Circuits for the Digital System
 
## Combinational circuits

- ◆ Logic circuits whose outputs at any time are determined *directly* and *only* from the present input combination
  - ▣ Memoryless





## Sequential circuits (Chapter 5)

- ◆ Circuits that employ **memory elements + (combinational) logic gates**
- ◆ Outputs are determined from the present input combination as well as the state of the memory cells

  
# Combinational Logic Circuits

- Memoryless:  $o=f(i)$

- Used for control, arithmetic, and data steering



 
- Combinational logic circuits are closed under **acyclic** composition



- Cyclic composition of two combinational logic circuits

- The **feedback** variable can remember the history of the circuits
- Sequential logic circuit

Acyclic

 

Cyclic

# Analysis Procedure

- ◉ Analysis for an available logic diagram
  - ◆ Make sure the given circuit is combinational
    - ▣ No *feedback path* or *memory element*
  - ◆ Derive the corresponding *Boolean functions*
  - ◆ Derive the corresponding *truth table*
  - ◆ Verify and analyze the design
    - ▣ Logic simulation (waveforms)
  - ◆ Explain the function


# Derivation of Boolean Functions (1/2)

- ⦿ Label all gate outputs that are functions of the input variables only. Determine the functions.
- ⦿ Label all gate outputs that are functions of the input variables and previously labeled gate outputs. And find the functions.
- ⦿ Repeat previous step until all the primary outputs are obtained.



# Derivation of Boolean Functions (2/2)

## Full adder example:

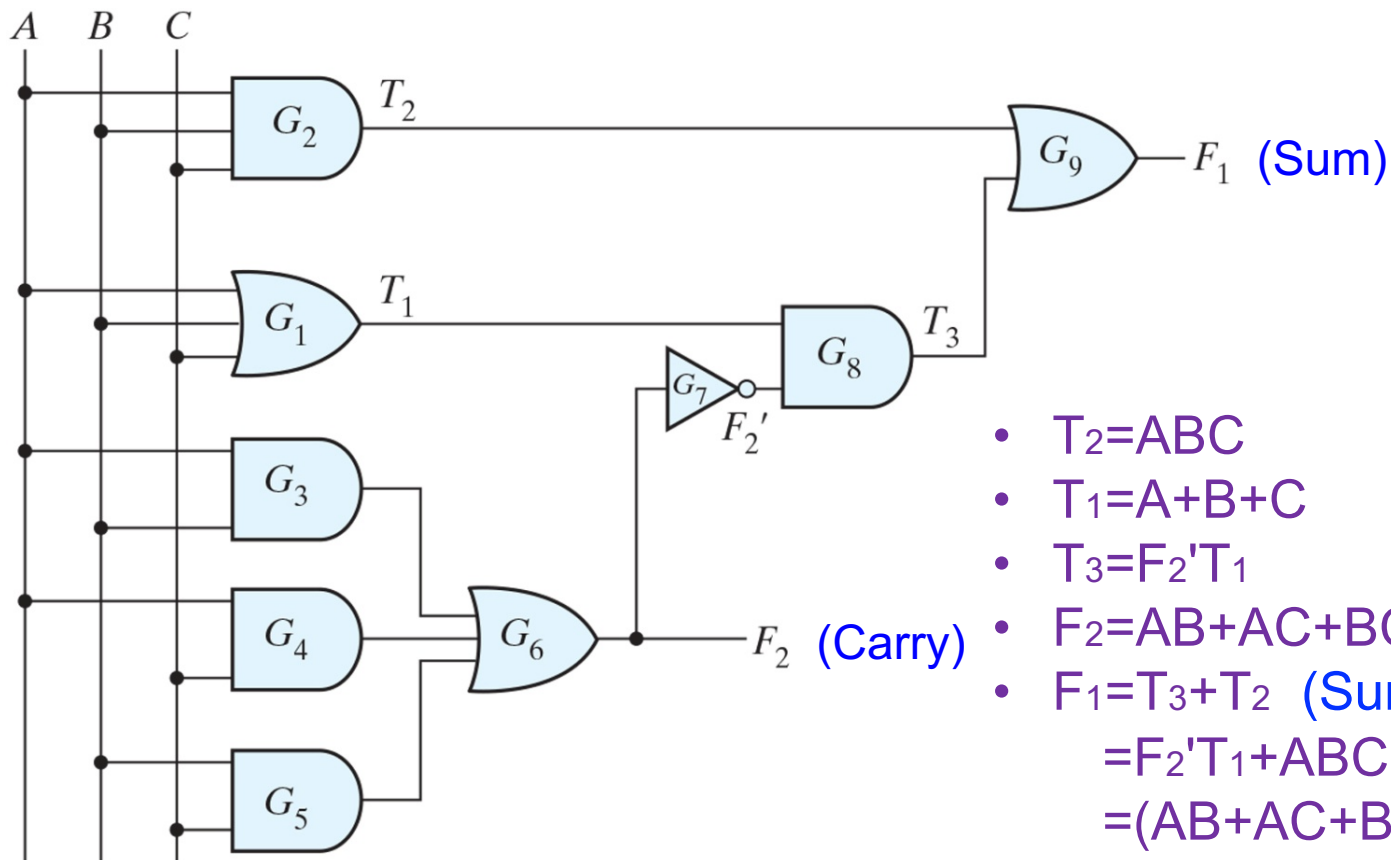

- $T_2 = ABC$
- $T_1 = A + B + C$
- $T_3 = F_2' T_1$
- $F_2 = AB + AC + BC$  (Carry)
- $F_1 = T_3 + T_2$  (Sum)  
 $= F_2' T_1 + ABC$   
 $= (AB + AC + BC)' (A + B + C) + ABC$   
 $= \underline{A'BC' + A'B'C + AB'C' + ABC}$

$$A \oplus B \oplus C$$

# Derivation of Truth Table (1/2)

## ⊙ For $n$ input variables

- ◆ List all the  $2^n$  input combinations from 0 to  $2^n - 1$
- ◆ Partition the circuit into small single-output blocks and label the output of each block
- ◆ Obtain the truth table of the blocks depending on the input variables only
- ◆ Proceed to obtain the truth tables for other blocks that depend on previously defined truth tables

# Derivation of Truth Table (2/2)

## Full Adder Example

			$AB+BC+AC$	$A+B+C$	$ABC$	$F_2' T_1$	$T_3+T_2$	
$A$	$B$	$C$	$F_2$	$F_2'$	$T_1$	$T_2$	$T_3$	$F_1$
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

# Design Procedure

## ① Specification

Spec

- ◆ From the specifications, determine the inputs, outputs, and their symbols

## ② Formulation

- ◆ Derive the truth tables (functions) from the relationship between the inputs and outputs

## ③ Optimization

- ◆ Derive the simplified Boolean functions for each output function

## ④ Technology mapping

- ◆ Derive the logic diagram based on the implementation technology

## ⑤ Verification

- ◆ Verify the design

# Code Conversion Example (1/3)

## BCD-to-excess-3 code converter

(1) Define the spec and IOs

(2) Derive truth table

①

Spec

- input (ABCD),  
output (wxyz)  
(MSB to LSB)
- ABCD: 0000~1001 (0~9)

②

Formulation

- $wxyz = ABCD + 0011$

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

# Code Conversion Example (2/3)

		C			
		CD			
		00	01	11	10
A	00	1			1
	01	1			1
	11	X	X	X	X
	10	1		X	X
		D			

$z = D'$

		C			
		CD			
		00	01	11	10
A	00	1		1	
	01	1		1	
	11	X	X	X	X
	10	1		X	X
		D			

$y = CD + C'D'$

## ③ Optimization:

- Determine simplified Boolean function

- $z = D'$
- $y = CD + \overbrace{C'D'}^{(C+D)'}$
- $x = B'C + B'D + BC'D'$
- $w = A + BC + BD$

7 ANDs, 3 ORs, 3 INVs

		C			
		CD			
		00	01	11	10
A	00		1	1	1
	01	1			
	11	X	X	X	X
	10		1	X	X
		D			

$$X = B'C + B'D + BC'D'$$

		C			
		CD			
		00	01	11	10
A	00				
	01		1	1	1
	11	X	X	X	X
	10	1	1	X	X
		D			


$$w = A + BC + BD$$

→ multi-level, non-standard

- $z = D'$
- $y = CD + (C + D)'$
- $x = B'(C + D) + B(C + D)'$
- $w = A + B(C + D)$

# Code Conversion Example (3/3)

## ④ Logic diagram

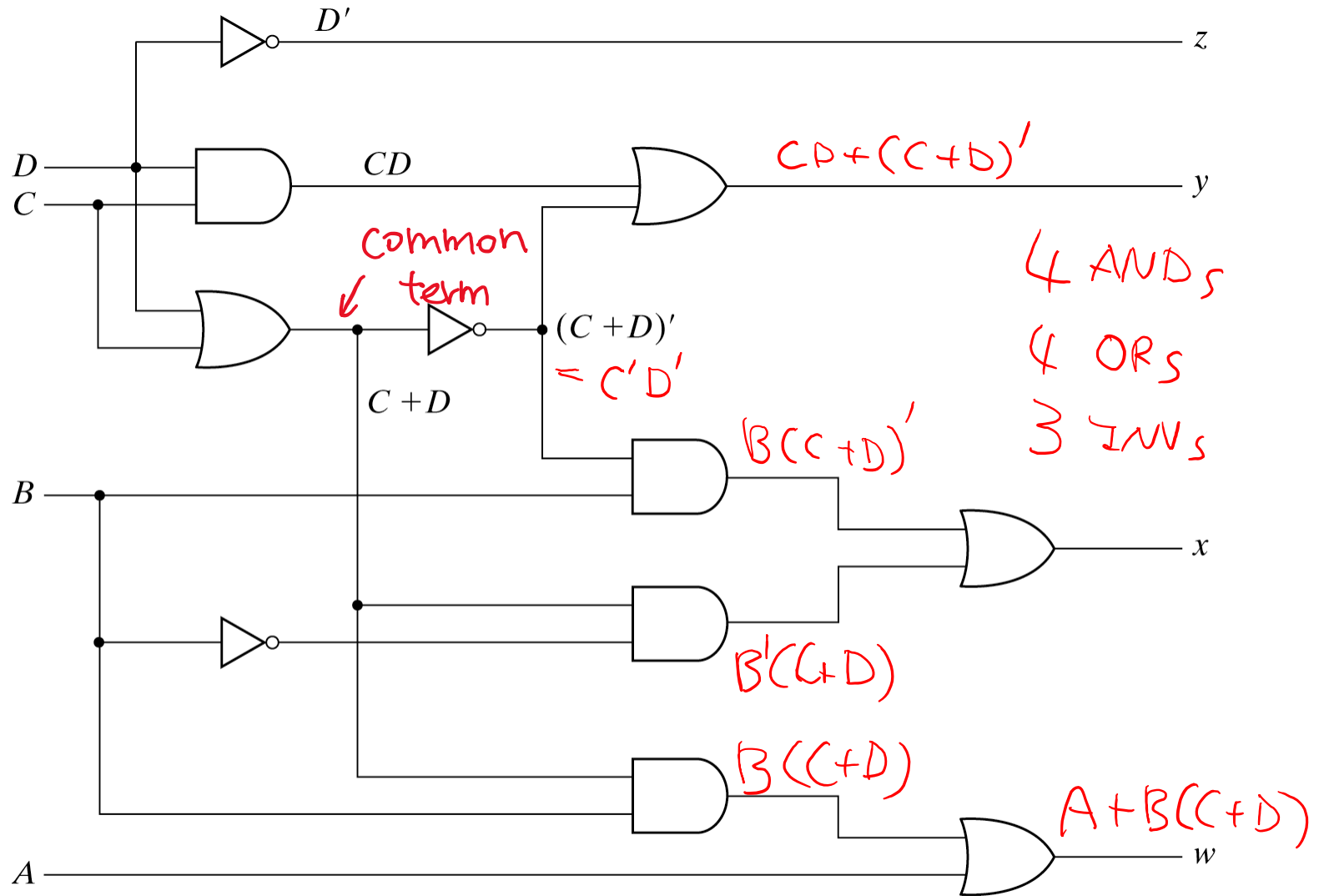

# Binary Adder-Subtractor



# Binary Half Adder (HA)


## IOs

- ◆ Input:  $x, y$
- ◆ Outputs:  $C$  (carry),  $S$  (sum)

## Truth table and functions


- ◆  $S = x'y + xy' = x \oplus y$
- ◆  $C = xy$

## Logic diagram

 

$$\begin{array}{r} x \\ + y \\ \hline C \ S \end{array}$$

$x$	$y$	$C$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

# Binary Full Adder (FA) (1/3)

## IOs

- ◆ Input:  $x, y, z$  (carry from previous lower significant bit)
- ◆ Outputs:  $C$  (carry),  $S$  (sum)

## Truth table

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{array}{r} x \\ y \\ + z \\ \hline CS \end{array}$$

		$yz$		$y$	
		00	01	11	10
$x$	0		1		1
$x$	1	1		1	

$z$

$$S = \sum(1, 2, 4, 7)$$

$$= x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = \sum(3, 5, 6, 7) = xy + yz + xz$$

		$yz$		$y$	
		00	01	11	10
$x$	0			1	
$x$	1		1	1	1



$z$

# Binary Full Adder (FA) (2/3)

## 2-level logic diagram

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + yz + xz$$

  



# Binary Full Adder (FA) (3/3)

- Full adder implemented with half adders
  - Two half adders and one OR gate

$$S = (x \oplus y) \oplus z$$

$$C = x'yz + xy'z + (xyz' + xyz)$$



$$= (x \oplus y)z + xy$$

  

# Binary (Ripple-Carry) Adder (1/2)



- Produces arithmetic sum of two binary numbers

Subscript i:	3	2	1	0	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

 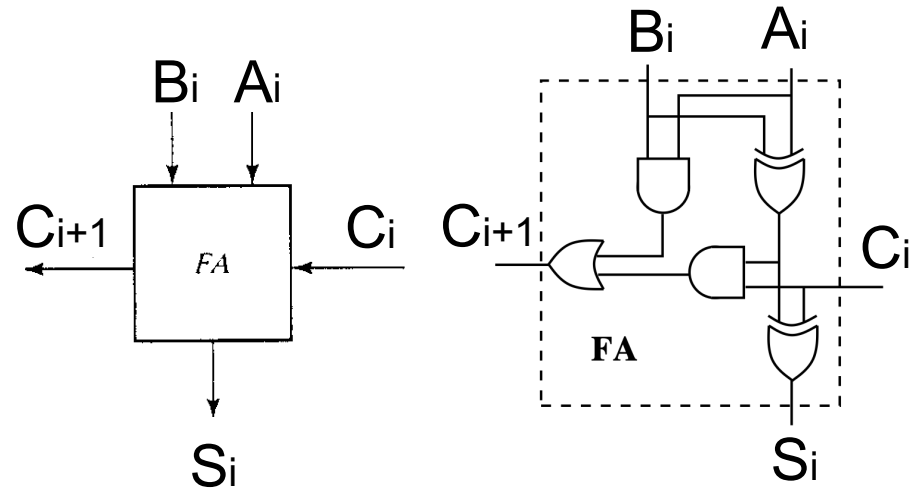
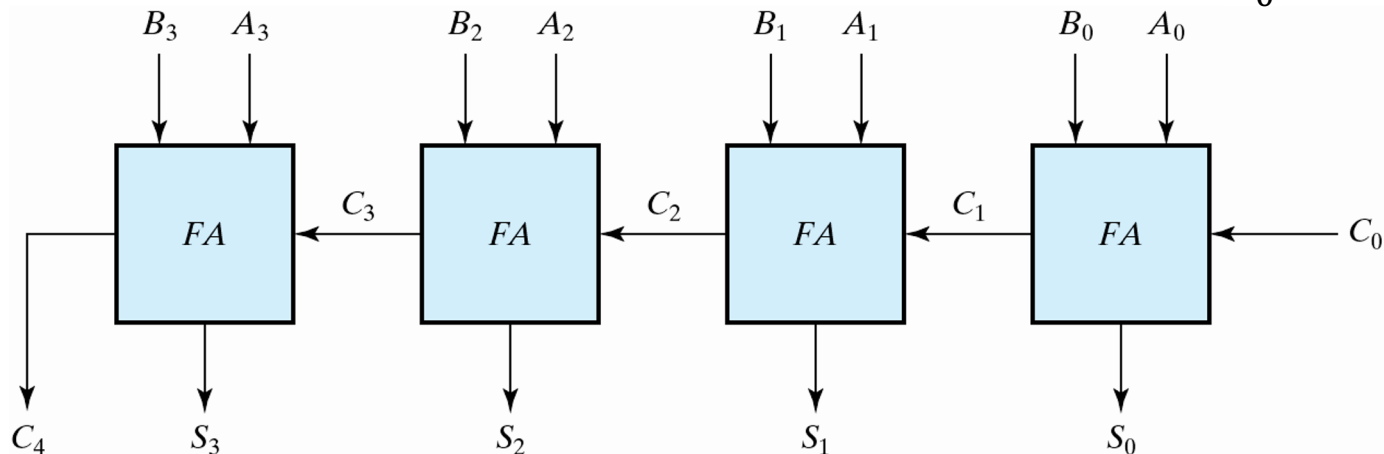 
# Binary (Ripple-Carry) Adder (2/2)

- ⊙ The computation time of a ripple-carry adder grows linearly with word length  $n$ 
  - ◆  $T=O(n)$  due to carry chain




# Carry Propagation
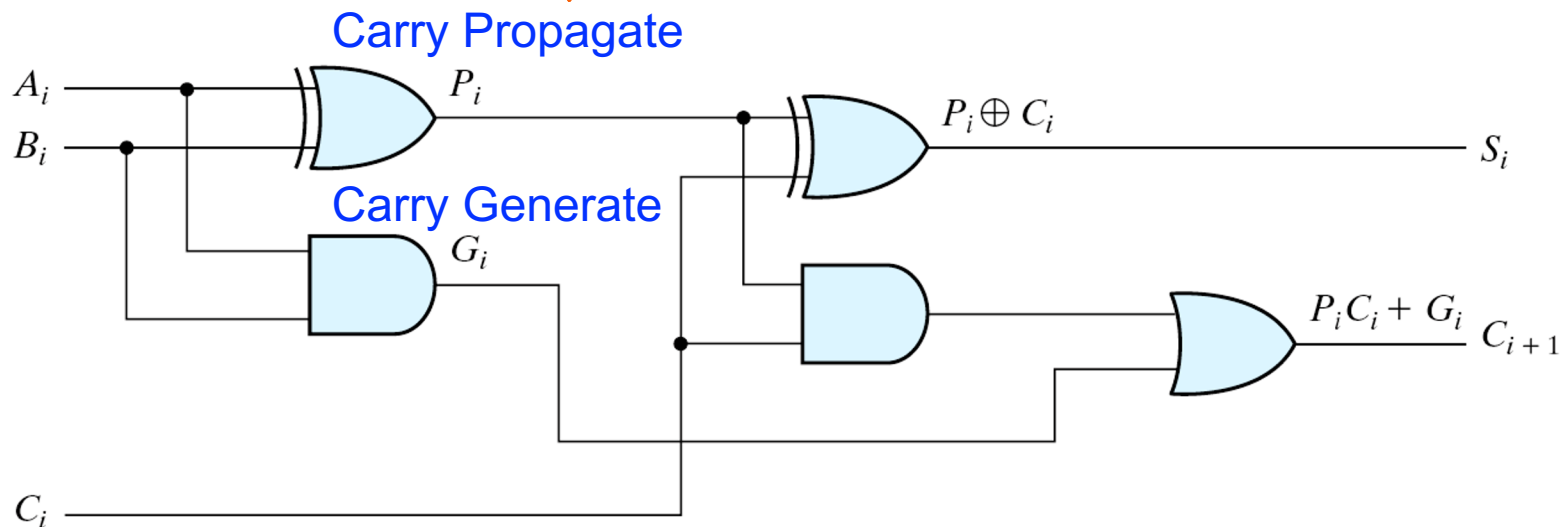
## For ripple carry adder

- ◆ Longest propagation delay:  $C_0 \rightarrow C_1 \rightarrow C_2 \rightarrow C_3 \rightarrow C_4$
- ◆ 8 gate levels (for 4-bit adder)
- ◆  $2n$  gate levels for the carry to propagate from input to output for an  $n$ -bit adder

*2n gate delays  $\Rightarrow$  carry propagation*



# Carry Lookahead Adder (CLA) (1/5)

- ◉ Reduce the carry propagation delay
  - ◆ Using faster gates
  - ◆ Parallel adders, e.g., the *carry lookahead adder (CLA)*

- ◉ Carry Lookahead Adder (CLA)

- ◆ Carry propagate:  $P_i = A_i \oplus B_i$

- ◆ Carry generate:  $G_i = A_i B_i$

- ◆ Sum:  $S_i = P_i \oplus C_i$

- ◆ Carry:  $C_{i+1} = G_i + P_i C_i$

- ◆  $C_1 = G_0 + P_0 C_0 = A_0 B_0 + (A_0 \oplus B_0) C_0$

- ◆  $C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$

- ◆  $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

