 


# Encoders

# Encoder (1/3)

- An encoder is an inverse of a decoder
  - ◆ Converts a **one-hot** input signal to a binary-encoded output signal
  - ◆ Other input patterns are forbidden in the truth table
- Example: a 4-to-2 encoder

a3	a2	a1	a0	b1	b0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1



$$b_0 = a_3 + a_1$$

$$b_1 = a_3 + a_2$$

# Encoders (2/3)

- ⦿ A combinational logic that performs the inverse operation of a decoder

- ◆ Only one input has value 1 at any given time
- ◆ Can be implemented with OR gates

8-to-3 encoder

$$X = D_4 + D_5 + D_6 + D_7$$


$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

Truth Table of an Octal-to-Binary Encoder

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

# Encoders (3/3)

 

## Limitations

Illegal Inputs

- When both  $D_3$  and  $D_6$  go high, output will be 111 → ambiguity
- Use priority encoder!



# Priority Encoders (1/2)

- Ensure only one of the input is encoded
- $D_3$  has the highest priority, while  $D_0$  has the lowest priority
- X is the don't care conditions
- V is the valid output indicator

status flag

Truth Table of a Priority Encoder

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

2 minterms  
4  
8

don't care

valid

# Priority Encoders (2/2)



		00	01	$D_2$		11	10	
$D_0$	00	X	1	1	1			
	01		1	1	1			
	11		1	1	1			
	10		1	1	1			
			$D_3$					

		00	01	$D_2$		11	10	
$D_0$	00	X	1	1	1			
	01	1	1	1	1			
	11	1	1	1	1			
	10		1	1	1			
			$D_3$					

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D_2'$$
  
$$V = D_0 + D_1 + \frac{(D_2 + D_3)}{x}$$



# Multiplexer



# Multiplexers

- ⊙ A multiplexer (or MUX) selects (usually by  $n$  select lines) binary information from one of many (usually  $2^n$ ) input lines and directs it to a single output line
- ⊙ 2-to-1 MUX (2:1 MUX)

$S$	$Y$
0	$I_0$
1	$I_1$

$$Y = S'I_0 + SI_1$$

if ( $S$ )  $Y = I_1$   
else  $Y = I_0$

  




# 4-to-1-line MUX

$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$


 
$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$



# Quadruple 2-to-1-line MUX



Function table		
$E$	$S$	Output $Y$
1	$X$	all 0's
0	0	select $A$
0	1	select $B$

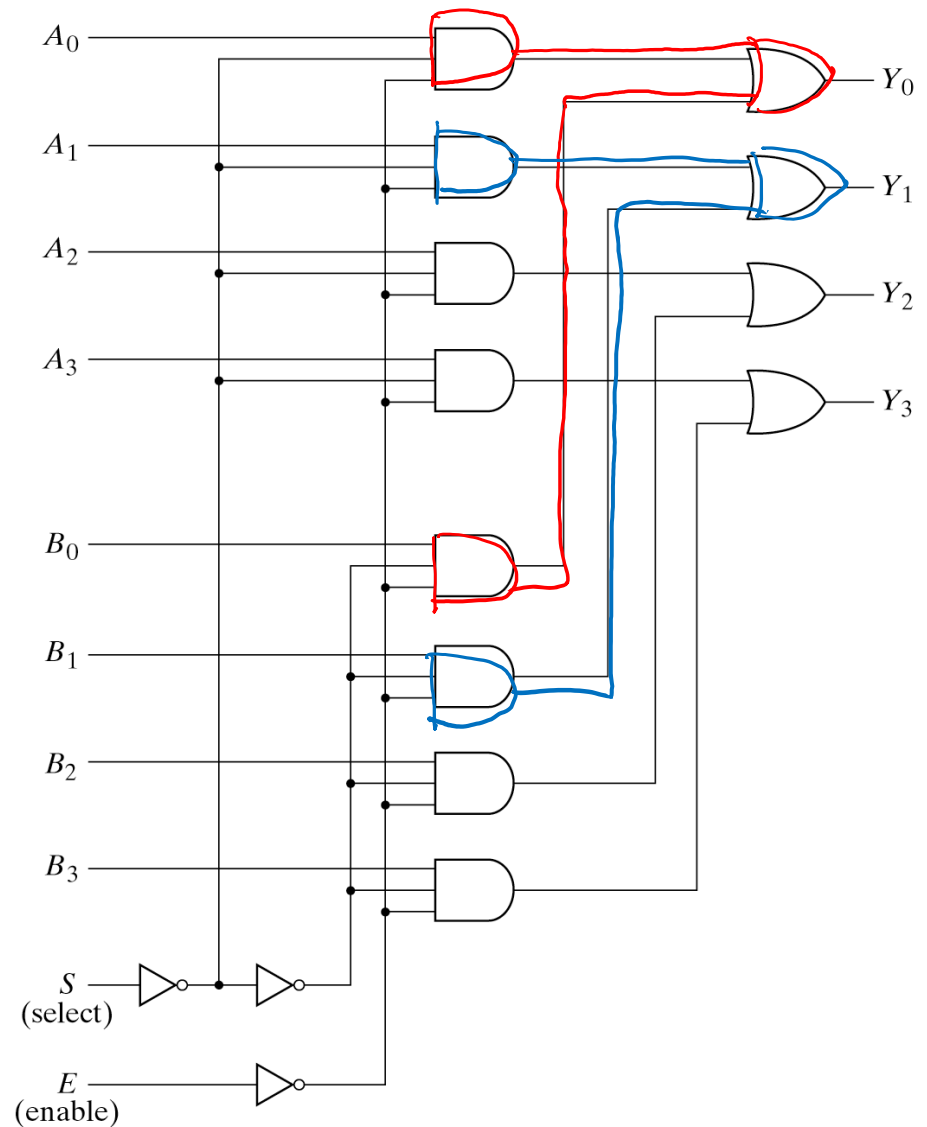 Two 4-bit vectors  
 $\Rightarrow$  4 2-to-1 MUXes


  
# Boolean Function Implementation (1/4)


- MUX: decoder + OR gate
- $2^{n-1}$ -to-1 MUX can implement any Boolean function of  $n$  input variable



# Boolean Function Implementation (2/4)

- Example:  $F(x, y, z) = \sum(1, 2, 6, 7)$

$$S = \sum(1, 2, 4, 7)$$

 

# Boolean Function Implementation (3/4)

- For an  $n$ -variable function
- Assign an ordering sequence of the  $n - 1$  input variables to the selection input of MUX
- The last (rightmost) variable will be used for the input lines
- Construct the truth table
- Consider a pair of consecutive minterms starting from  $m_0$
- Determine the input lines according to the last variable and output signals in the truth table

$2^{n-1} - 1$




# Boolean Function Implementation (4/4)

Example:  $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$

Select

A	B	C	D	F	
0	0	0	0	0	
0	0	0	1	1	$F = D$
0	0	1	0	0	
0	0	1	1	1	$F = D$
0	1	0	0	1	
0	1	0	1	0	$F = D'$
0	1	1	0	0	
0	1	1	1	0	$F = 0$
1	0	0	0	0	
1	0	0	1	0	$F = 0$
1	0	1	0	0	
1	0	1	1	1	$F = D$
1	1	0	0	1	
1	1	0	1	1	$F = 1$
1	1	1	0	1	
1	1	1	1	1	$F = 1$

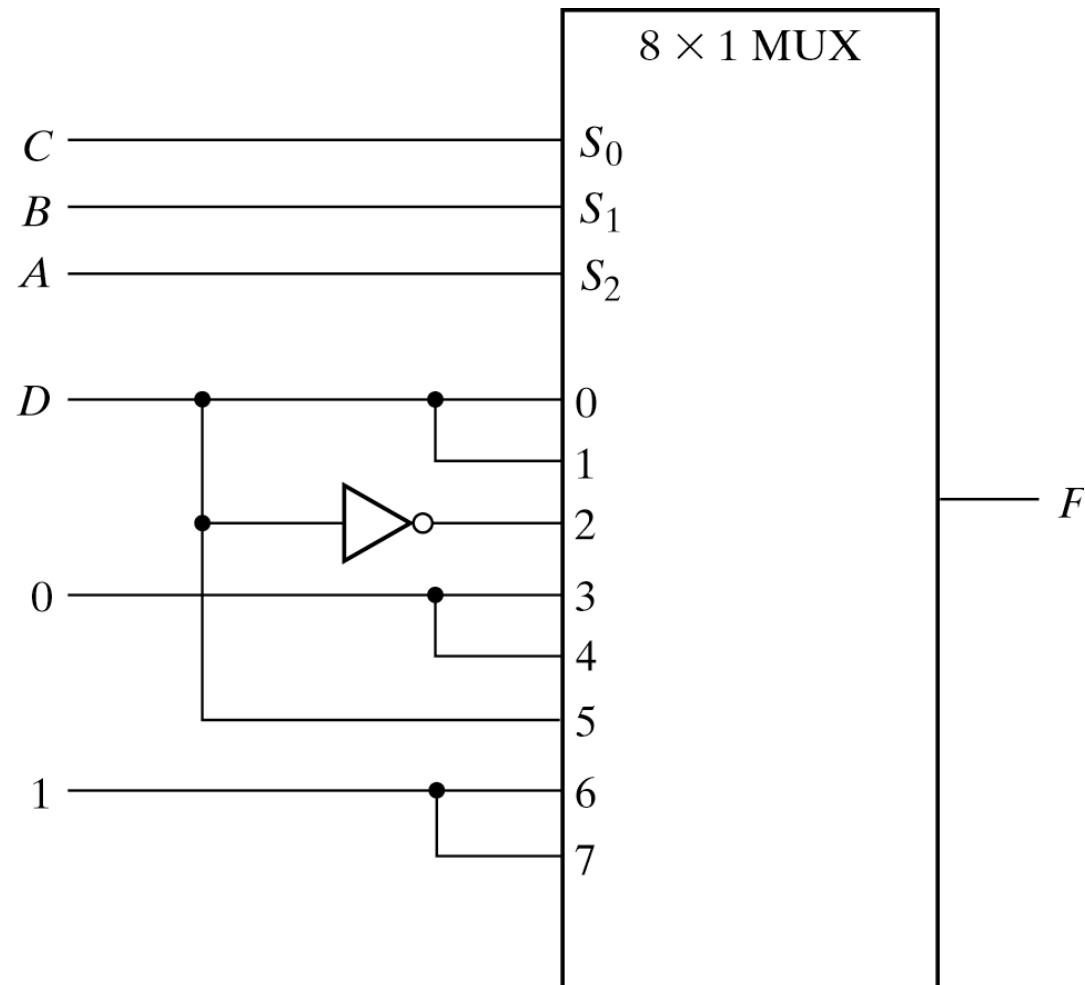


# Three-State Gates

( Tri-state )

# Three-State Gates (1/2)

 

- ⦿ A multiplexer can be constructed with three-state gates
- ⦿ Output states: 0, 1, and Z (high-impedance, or open circuits)






$C$	$Y$
0	<b>Z</b>
1	<b>A</b>

- ⦿ Three-state gates can be used to build up a *bus*
  - ◆ A communication channel among different modules in a digital system



   $G = 1 \quad \emptyset$   
 nMOS  on off  
 $G = \emptyset \quad 1$   
 pMOS  off on



$C = 1, Y = A'$

$C = \emptyset, Y = \text{hi-z}$

high-z

high-impedance

# Three-State Gates (2/2)

- Examples: multiplexers with three-state gates

